

Big Muff


Variant: Final Version

2025-05-22


Rev Final Version

Page	Index	Page	Index	Page	Index	Page	Index
1	Cover Page	11		21		31	
2	Project Architecture	12		22		32	
3		13		23		33	
4		14		24		34	
5		15		25		35	
6		16		26		36	
7		17		27		37	
8		18		28		38	
9		19		29		39	
10		20		30		40	

TOP VIEW

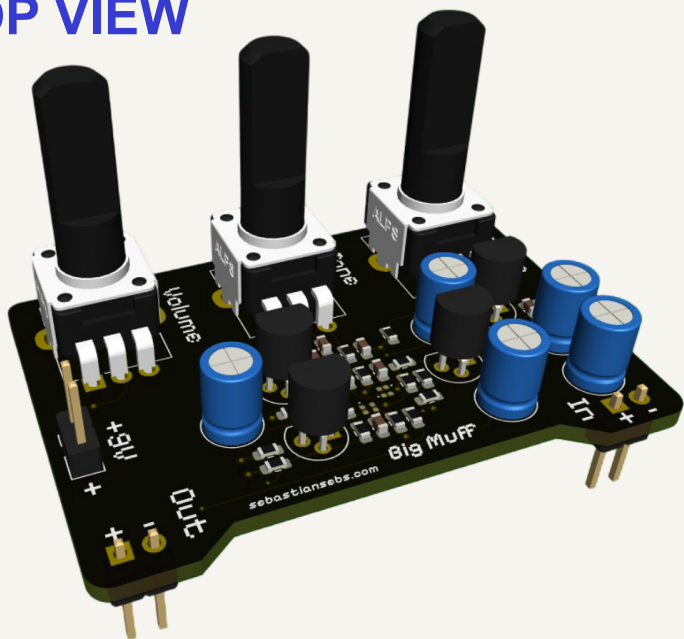

BOTTOM VIEW

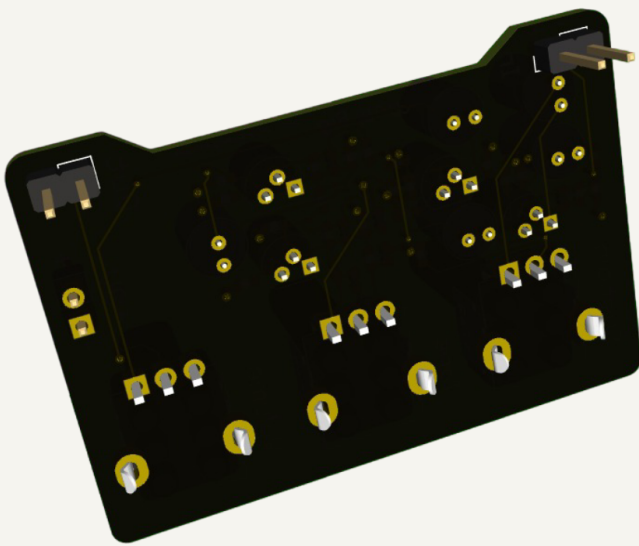

DISCLAIMER

This project implements a classic Big Muff Pi guitar fuzz pedal, featuring BJT-based amplification stages, and interactive tone shaping using potentiometers (Adjusts Volume, Tone, and Sustain).

For larger capacitance values (e.g., 1uF), we utilized electrolytic capacitors.
For smaller capacitance values (e.g., 470pF, 0.1uF, 0.0015uF, 0.015uF), film capacitors (such as polyester or metallized polypropylene) or ceramic capacitors are preferred.

Final Version 5/22/2025

DESIGN CONSIDERATIONS

DESIGN NOTE:

Example text for informational design notes.

DESIGN NOTE:

Example text for debug notes.

DESIGN NOTE:

Example text for cautionary design notes.

DESIGN NOTE:


Example text for critical design notes.

LAYOUT NOTE:


Example text for critical layout guidelines.

	Comments:		Company:		Variant:	
			sebastiansebs.com		Final Version	
			Board Name:		Project Name:	
	Sheet Title:		Big Muff		Big Muff	
	File Name:		Big Muff.kicad_sch		Designer:	
					Sebastian Silva	
	Sheet Path:		-		Date:	
					5/22/2025	
					Revision:	
					Final Version	
					Size:	
					A3	
					Sheet:	
					1 of 2	

[2] Project Architecture

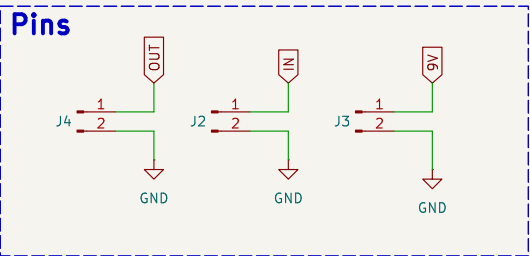


Input Buffer (Pre-Amplifier)

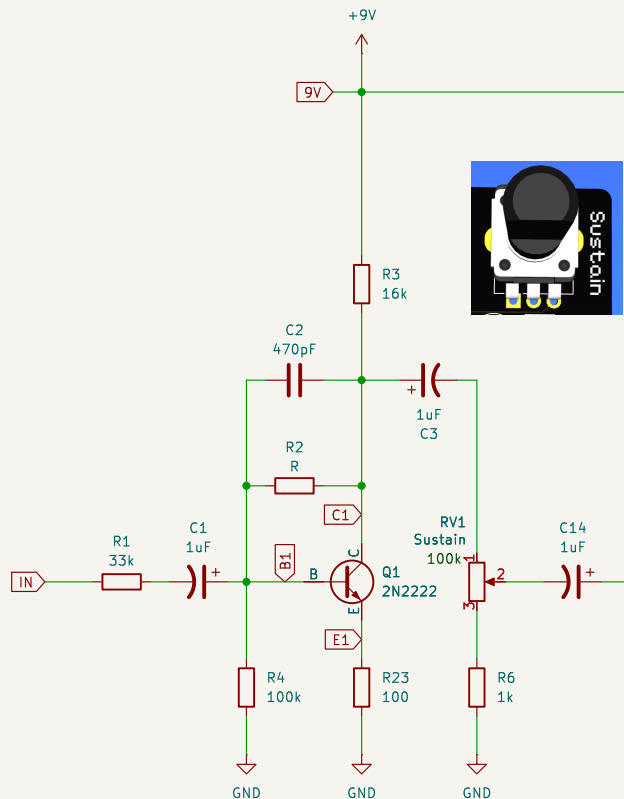


This stage acts as a pre-amplifier/buffer.

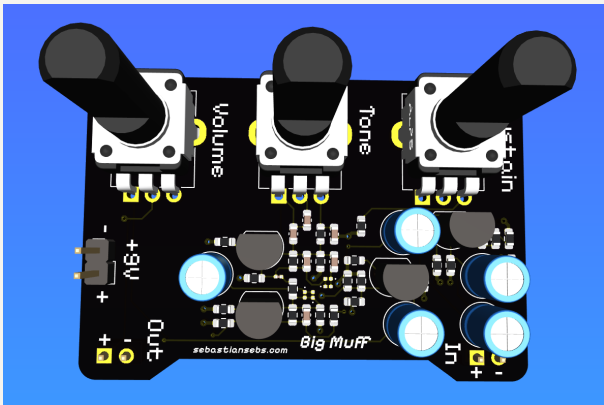The large input resistor R1, along with C1, helps present a high input impedance to the guitar signal. Q1 amplifies the signal, and the emitter resistor R23 (bypassed by C3 for AC) provides stability. C2 and R2 form a filter that shapes the tone early on. The amplified signal is then coupled via C14 to the next stage.



Clipping Stage

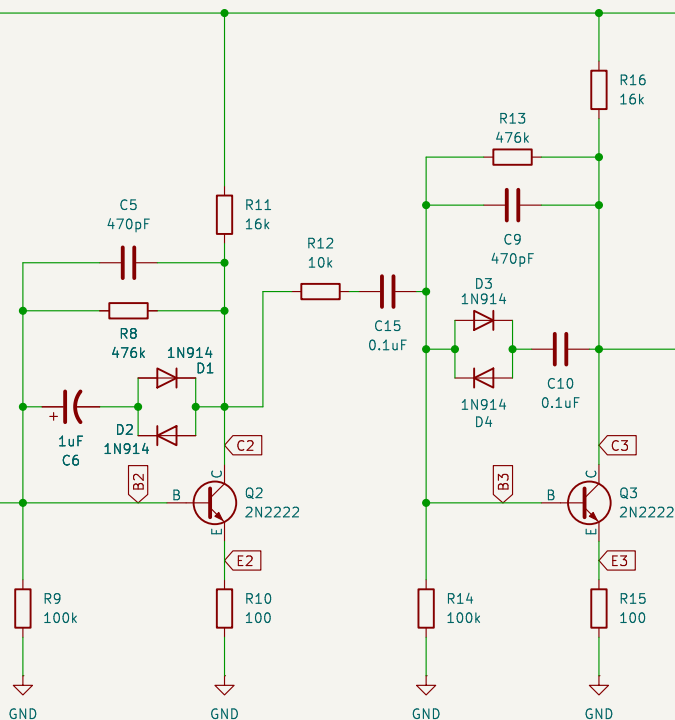


The Gain/Clipping part is divided by 2 stages:

For the first Transistor stage. Q2 provides significant amplification.

The diodes D1 and D2 are placed in a feedback loop (or across the signal path in some variations) to clip the amplified signal when it reaches a certain voltage threshold, producing the characteristic Big Muff distortion. The resistors R5, R6, R7, and R8 set the bias for Q2. C7 bypasses R9 for maximum AC gain.


Tone Control

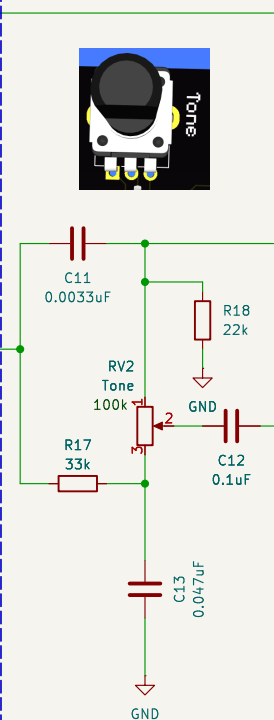

This is the passive "Tone" control section of the Big Muff.


It's a variable low-pass/high-pass filter. As you turn RV2, it shifts the frequency response, allowing sweeping between more bassy (less treble) and more trebly (less bass) sounds.

Output Buffer (Volume Control)

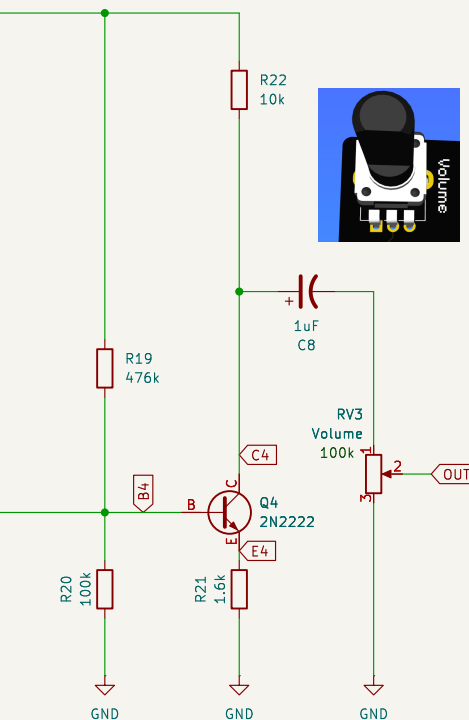

This final stage acts as an output buffer and incorporates the master volume control.

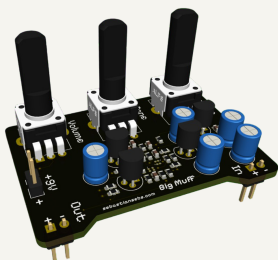Q4 provides a final stage of amplification and buffering to drive the output effectively. The volume control (RV3) is placed at the output of this stage, allowing you to adjust the overall loudness of the distorted signal.



Comments:	Company: sebastiansebs.com		Variant: Final Version	
	Board Name: Big Muff		Project Name: Big Muff	
Sheet Title: Project Architecture	File Name: Project Architecture.kicad_sch	Designer: Sebastian Silva	Date: 5/22/2025	Revision: Final Version
Sheet Path: /Project Architecture/	Reviewer: -	Size: A3	Sheet: 2 of 2	